

Lab2 Notes

zjx@ustc.edu.cn

2019.4.4

REG型变量

- 申明为reg型的变量，综合后不一定生成寄存器！

```
wire [7:0] a, b;  
reg [7:0] r1, r2, r3;
```

```
always @(*) // (en, a, b)  
    if (en) r1 = a;  
    else r1 = b;
```

```
always @(en, a) // @(*)  
    if (en) r2 = a;
```

```
always @(posedge clk)  
    if (en) r3 = a;
```

组合电路：

敏感变量不要遗漏



所有分支均有赋值

不能含反馈，如 $r1=r1+1$

锁存器：尽量避免使用



寄存器：必有触发时钟

示例：三个数排序

 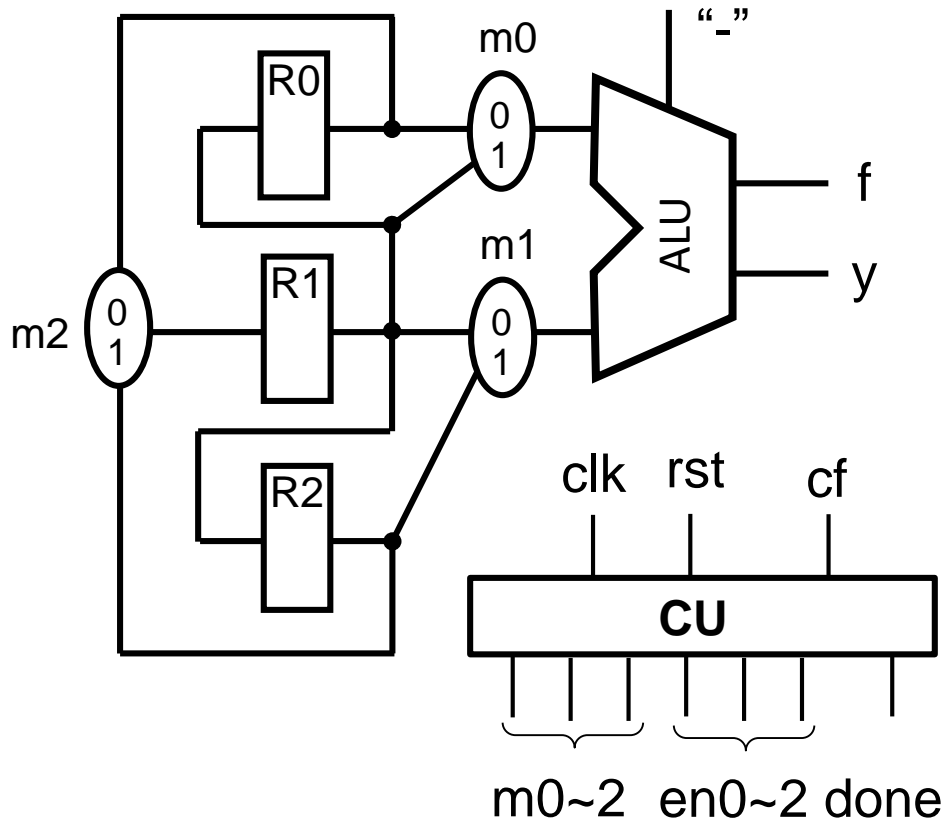

思考题：如何优化？

示例：三个数排序


 
 


FSM描述方式

一段式

两段式

三段式

   

示例：三个数排序 (续1)

```
wire [4:0] i0, i1, i2, r0, r1, r2, a;
```

```
// Data Path
```


```
register R0 (i0, en0, rst, clk, r0),  
        R1 (i1, en1, rst, clk, r1),  
        R2 (i2, en2, rst, clk, r2);
```

```
alu ALU (a, r1, SUB, cf);
```

```
mux M0 (m0, r0, r2, a),  
    M1 (m1, x0, r1, i0),  
    M2 (m2, a, x1, i1),  
    M3 (m3, r1, x2, i2);
```

```
// Control Unit
```
 
```
always @(posedge clk, posedge rst)  
    if (rst) current_state <= LOAD;  
    else  
        current_state <= next_state;
```



```
always @(*) begin  
    case (current_state)  
        LOAD: next_state = CX01;  
        CX01: next_state = CX12;  
        CX12: next_state = CX01S;  
        CX01S: next_state = HLT;  
        HLT: next_state = HLT;  
        default: next_state = HLT;  
    endcase  
end
```

示例：三个数排序 (续2)

// 两段式：控制信号--组合输出

```
always @(*) begin
```

```
    {m0, m1, m2, m3, en0, en1, en2, done} = 8'h0;
```

```
    case (current_state)
```

```
        LOAD: {m2, m3, en0, en1, en2} = 5b'11111;
```

```
        CX01, CX01S: begin m1 = 1; en0 = cf; en1 = cf; end
```

```
        CX12: begin m0 = 1; en1 = ~cf; en2 = ~cf; end
```

```
        HLT: done = 1;
```

```
    endcase
```

```
end
```

// 三段式：控制信号--寄存器输出

```
always @(posedge clk, posedge rst) begin
```



```
    if (rst) {m1, m2, m3, en0, en1, en2, done} <= 7b'011_1110; // LOAD
```

```
    else case (next_state)
```

```
        CX01, CX01S: {m0, m1, m2, en0, en1, en2} <= {3b'010, cf, cf, 1'b0};
```



```
        .....
```

有何问题？如何解决？

  

示例：三个数排序 (续3)
  
```
// 将数据通路和控制信号合二为一
reg [4:0] r0, r1, r2;
always @(posedge clk, posedge rst) begin
  if (rst) begin
    r0 <= x0; r1 <= x1; r2 <= x2;
  end
  else
    case (state)
      CX01, CX01S:
        if (r1 > r0) begin r0 <= r1; r1 <= r0; end
      CX12:
        if (r2 > r1) begin r1 <= r2; r2 <= r1; end
      HLT: done <= 1;
    endcase
  end
end
```




下载时端口映射问题

- **Flow Navigator窗口 >> Project Manager >> Project Settings**

- General >>
- Project device


xc7a100tcsg324-1

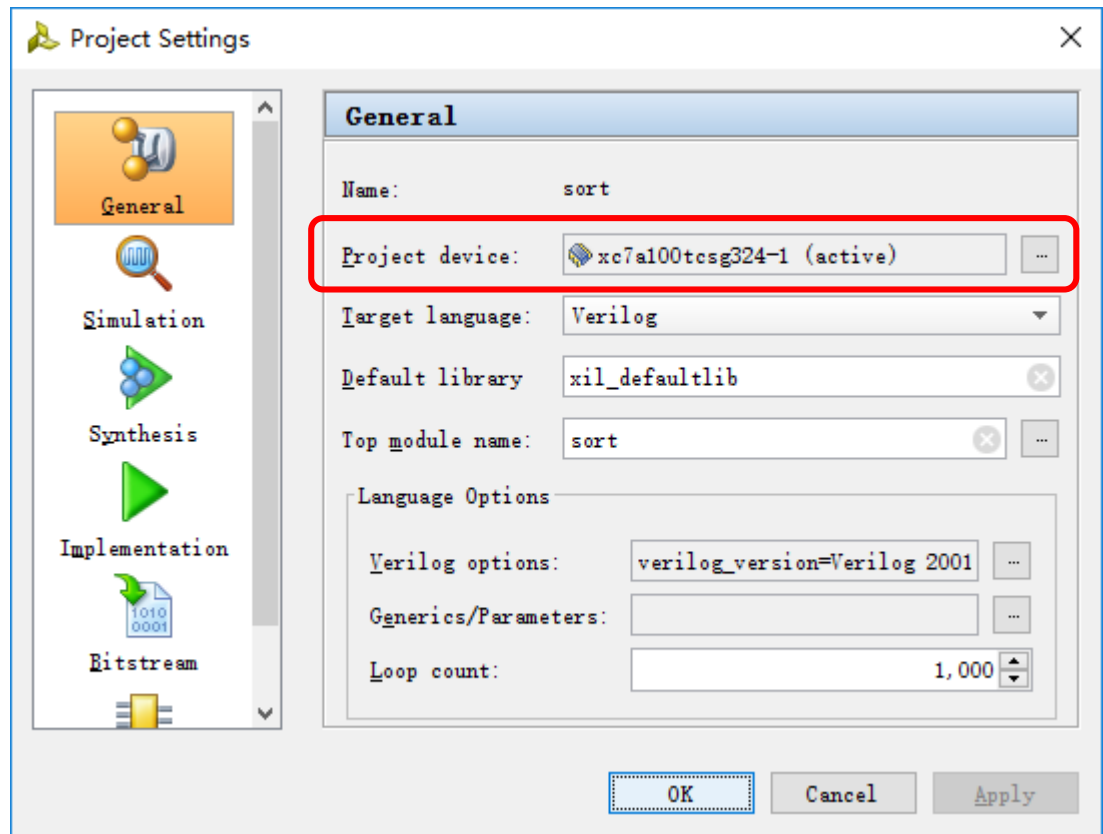

仿真时模块选择问题

- **Flow Navigator窗口 >> Project Manager >> Project Settings**

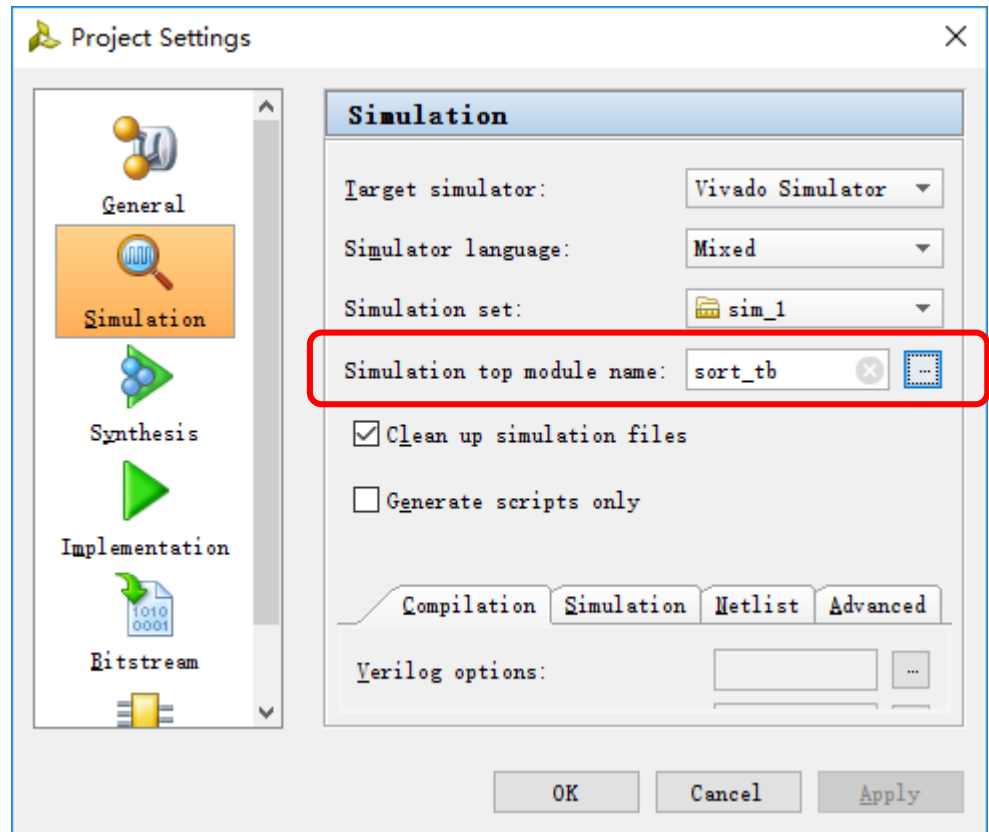- Simulation >>
- Simulation top module name



The End